







$$I = \frac{V}{R}$$

Worksheet - Series Circuit Problems, Episode 903 Name _____



Remember that in a series circuit:

- the current in every part of the circuit (is the same, adds up).
- the voltage supplied by the battery is the _____ voltage of the circuit, and the voltage drops across each resistor (is the same, adds up to) the total voltage.
- to calculate total resistance, (add, use reciprocals).
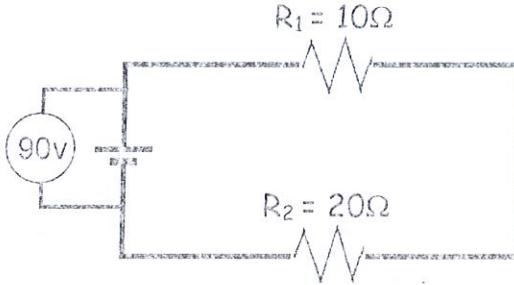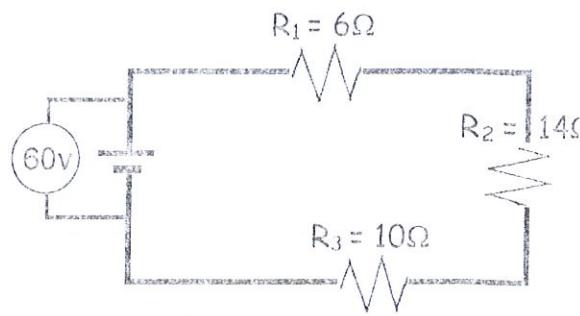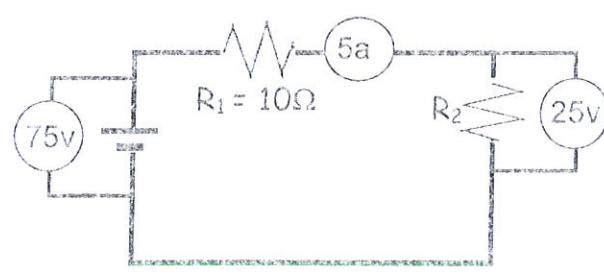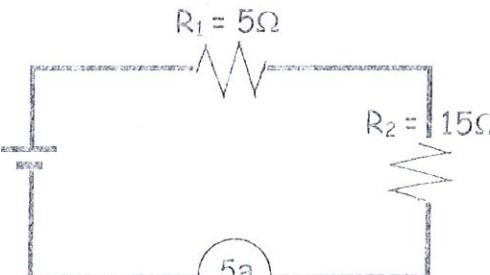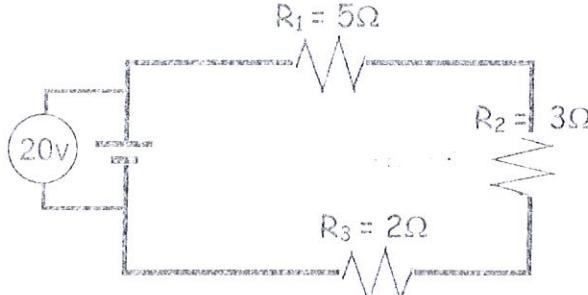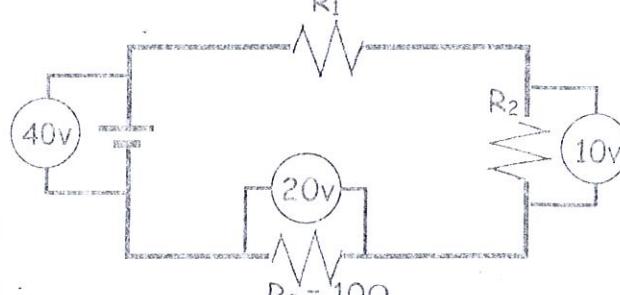
| | |
|--|--|
|  <p>$R_1 = 10\Omega$</p> <p>$R_2 = 20\Omega$</p> <p>$R_T = 30\Omega$ $I_T = 3a$ $I_1 = 3a$ $I_2 = 3a$ $V_1 = 30V$ $V_2 = 60V$</p> |  <p>$R_1 = 6\Omega$</p> <p>$R_2 = 14\Omega$</p> <p>$R_3 = 10\Omega$</p> <p>$R_T = 30\Omega$ $I_T = 2a$ $I_1 = 2a$ $I_2 = 2a$ $I_3 = 2a$ $V_1 = 12V$ $V_2 = 28V$ $V_3 = 20V$</p> |
|  <p>$R_1 = 10\Omega$</p> <p>$R_2 = 25V$</p> <p>$V_1 = 50V$ $I_2 = 5a$ $R_2 = 55\Omega$</p> |  <p>$R_1 = 5\Omega$</p> <p>$R_2 = 15\Omega$</p> <p>$V_1 = 25V$ $V_2 = 75V$ $V_T = 100V$</p> |
|  <p>$R_1 = 5\Omega$</p> <p>$R_2 = 3\Omega$</p> <p>$R_3 = 2\Omega$</p> <p>$R_T = 10\Omega$ $I_T = 2a$ $V_1 = 10V$ $V_2 = 6V$ $V_3 = 4V$</p> |  <p>R_1</p> <p>R_2</p> <p>$R_3 = 10\Omega$</p> <p>$I_3 = 2a$ $I_1 = 2a$ $V_1 = 10V$ $R_1 = 5\Omega$ $R_2 = 5\Omega$</p> |

